

# Contents

PREFACE	5
CONTENTS	6
SYMBOLS	10
1 D.C. CURRENTS AND D.C. VOLTAGES	13
1.1 Current, potential, voltage and resistance	13
1.2 The voltage source and the current source	15
1.3 Energy and power	17
1.4 Connection of resistors	18
1.5 Voltage and current division	18
1.6 The solution of larger networks	19
1.7 The mesh method	20
1.8 The node method	22
1.9 The current law for a cut-set	24
1.10 Superposition	24
1.11 Tellegen's theorem	26
1.12 Two-ports	28
1.13 Thévenin's and Norton's theorems	30
1.14 Maximum power transfer	32
1.15 Star-delta transformation	33
1.16 Controlled sources	34
1.17 Transactors	34
1.18 Special networks	37
1.19 Thévenin's theorem in networks with transactors	40
1.20 The operational amplifier	42
1.21 Problems	45
2 VARYING CURRENTS AND VOLTAGES	59
2.1 Introduction	59
2.2 Direction and polarity	59
2.3 Kirchhoff's laws and Ohm's law	60
2.4 Periodical quantities	60
2.5 Average value	60
2.6 Power	60
2.7 Effective value	61
2.8 Sinusoidal quantities	62
2.9 Power for sinusoidal voltages and currents	64
2.10 The sum of two sinusoidal quantities	66

2.11	The capacitor	66
2.12	The inductor	67
2.13	Energy stored in capacitor and inductor	68
2.14	The passive elements in sinusoidal excitation	69
2.15	A larger network in sinusoidal excitation	70
2.16	Complex numbers	74
2.17	Operations with complex numbers	75
2.18	Complex voltages and currents	76
2.19	Kirchhoff's laws for complex quantities	83
2.20	The complex $\phi$ time transformation	88
2.21	Vector diagrams	92
2.22	Complex power	96
2.23	Maximum power transfer for complex quantities	100
2.24	Problems	101
3	SOME PROPERTIES OF NETWORKS	115
3.1	Polar diagrams	115
3.2	Bode diagrams	122
3.3	Duality	128
3.4	Resonance	130
3.5	Lossless one-ports	138
3.6	Zobel networks	145
3.7	Problems	147
4	MAGNETIC COUPLED INDUCTORS, TRANSFORMERS	155
4.1	Introduction	155
4.2	Mutual induction	155
4.3	Current direction, voltage polarity and the mode of winding	157
4.4	The value of $ M $	158
4.5	Hopkinson's formula	160
4.6	The transformer	161
4.7	Impedance transformation	164
4.8	Equivalent circuits for magnetic coupled coils	166
4.9	The voltage and the current transformer	168
4.10	Problems	169
5	THREE-PHASE SYSTEMS	175
5.1	The rotating field	175
5.2	The creation of a rotating field	176
5.3	The principle of the three-phase motor	176
5.4	The principle of the three-phase generator	178
5.5	The three-phase supply	178
5.6	Complex three-phase voltages	180
5.7	The three-phase load	180

## 8 *Electrical Networks*

5.8	Power in three-phase systems	184
5.9	Phase compensation	185
5.10	Problems	188
6	FOURIER SERIES	195
6.1	Introduction	195
6.2	The infinity series of Fourier	196
6.3	The frequency spectrum	198
6.4	Dirichlet's conditions	200
6.5	Gibb's phenomenon	200
6.6	The Fourier series in complex form	203
6.7	The finite Fourier series	205
6.8	Reflections on symmetry	208
6.9	The effective value of a Fourier series	210
6.10	Problems	212
7	THE COMPLEX FREQUENCY	217
7.1	Introduction	217
7.2	A capacitor discharges over a resistor	217
7.3	A capacitor discharges over an inductor with series resistor	219
7.4	The complex frequency plane	223
7.5	Extension of the meaning of impedance	224
7.6	Kirchhoff's laws if the frequency is complex	226
7.7	Poles and zeros	228
7.8	Frequency characteristics	230
7.9	The coincidence of poles and zeros	234
7.10	The order of a network	235
7.11	Natural oscillations of a one-port	236
7.12	The location of the poles and zeros for an immittance	239
7.13	The number of poles for an immittance	240
7.14	Poles and zeros on the imaginary axis	240
7.15	The amplitude surface	241
7.16	Problems	243
8	TWO-PORTS, FILTERS	251
8.1	Introduction	251
8.2	Two-port matrices	251
8.3	Interconnection of two-ports	256
8.4	Reciprocity	260
8.5	Restoring the port condition	262
8.6	Poles and zeros of a transfer function	264
8.7	Once more the operational amplifier (opamp)	265
8.8	The realisation of differential equations	268
8.9	Filters	270

8.10	Problems	274
9	NETWORKS CONTAINING SWITCHES	283
9.1	Introduction	283
9.2	Discontinuity	283
9.3	The continuity theorem	284
9.4	Initial conditions	286
9.5	A second-order transient problem	287
9.6	Natural oscillations	291
9.7	The impulse function	291
9.8	Sine and cosine functions with decreasing amplitude	294
9.9	Summarising example	296
9.10	Conclusion	300
9.11	Problems	301
10	COMPUTER AIDED ANALYSIS	305
10.1	Introduction	305
10.2	The NA-matrix	305
10.3	The concept ‘stamp’	306
10.4	The MNA-matrix	306
10.5	Outline of the stamps	307
10.6	Earthing a terminal	315
10.7	Connecting two terminals	316
10.8	A terminal becomes an internal node	317
10.9	Examples	318
10.10	The solution of the matrix equation	318
10.11	Numerical integration	319
10.12	Equivalent circuits	324
10.13	Nonlinear elements	337
10.14	Problems	344
	APPENDICES	353
	Appendix I Linearity and superposition	353
	Appendix II Tellegen’s theorem	357
	Appendix III Reciprocity	359
	Appendix IV Thévenin’s and Norton’s theorems	363
	Appendix V Star-delta transformation	368
	Appendix VI Foster’s theorem	371
	ANSWERS TO PROBLEMS	379
	INDEX	413